

Microelectronics Circuit

Evolution of Electronic Devices

Vacuum
Tubes



(a)

Discrete
Transistors



(b)

Integrated
Circuits



(c)

Surface-Mount
Circuits




(d)

Transistors and Moore's Law


- Transistor: The fundamental building block of modern electronic devices.
 - Moore's Law: the number of transistor that can be placed inexpensively on an integrated circuit die **doubles** every 18 months.
-

Transistors and Moore's Law

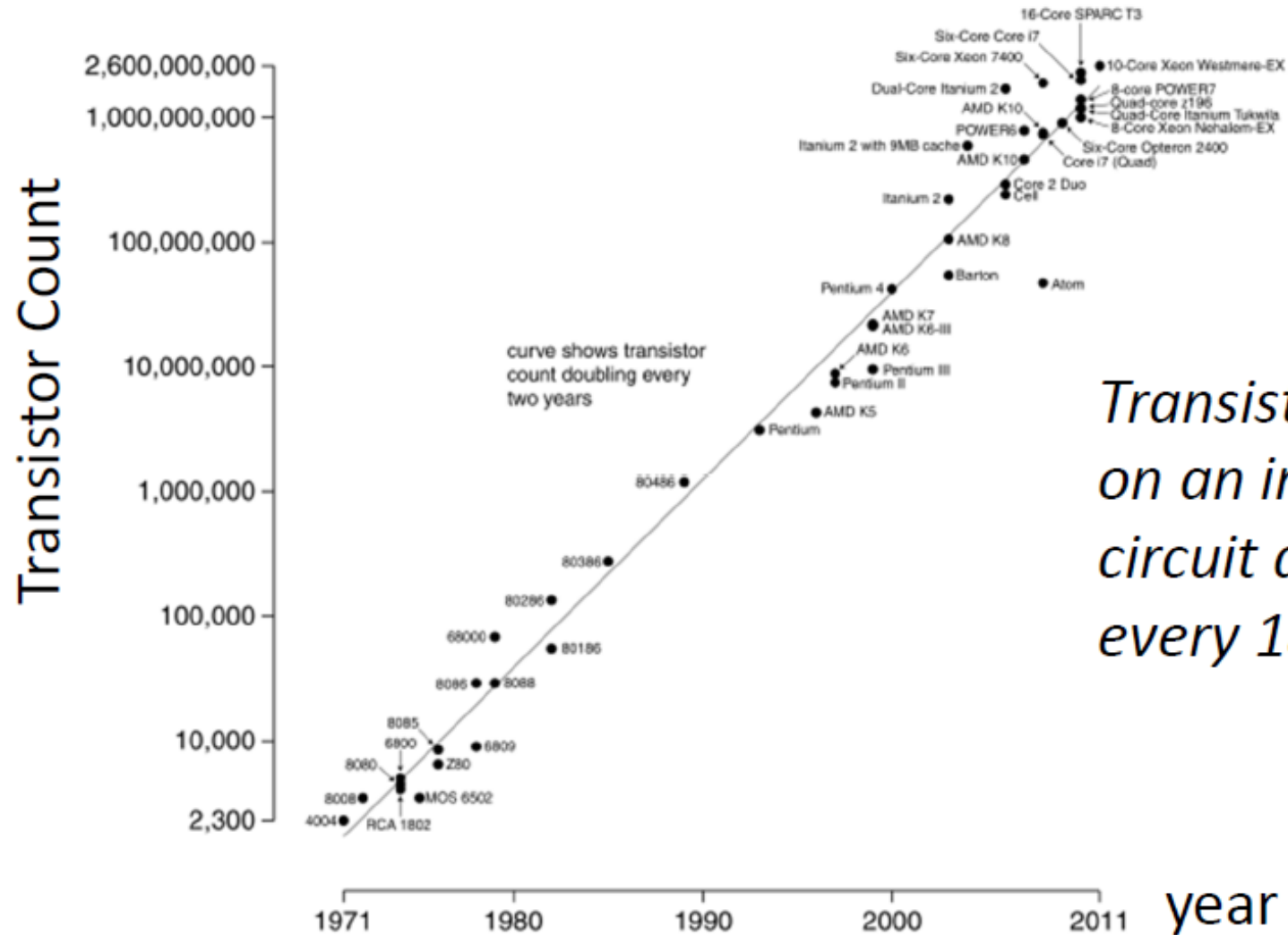


number of transistors

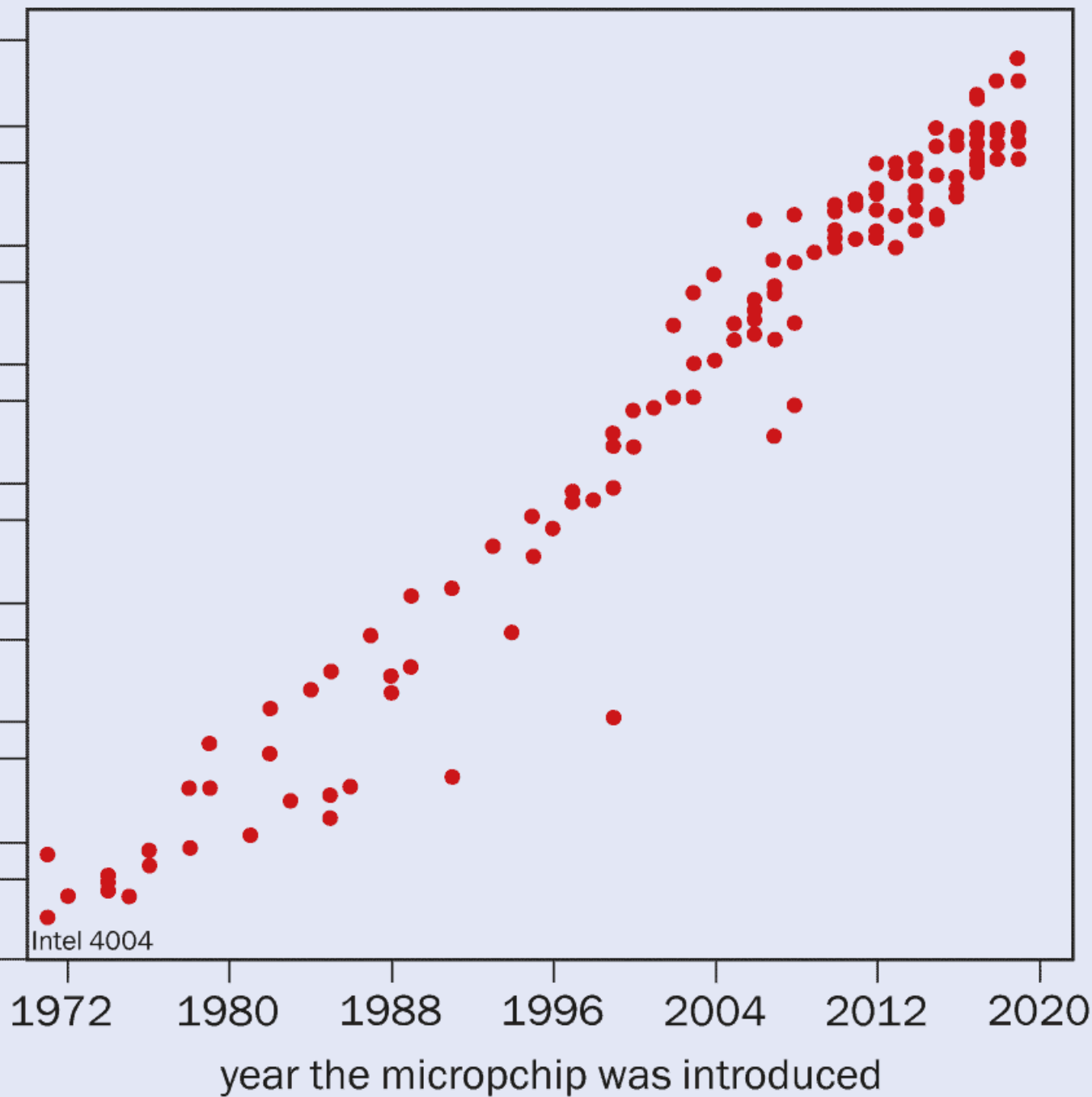50,000,000,000
10,000,000,000
5,000,000,000
1,000,000,000
500,000,000
100,000,000
50,000,000
1,000,000
500,000
1,000,000
500,000
100,000
50,000
10,000
5,000
1,000




Minimum Feature Size

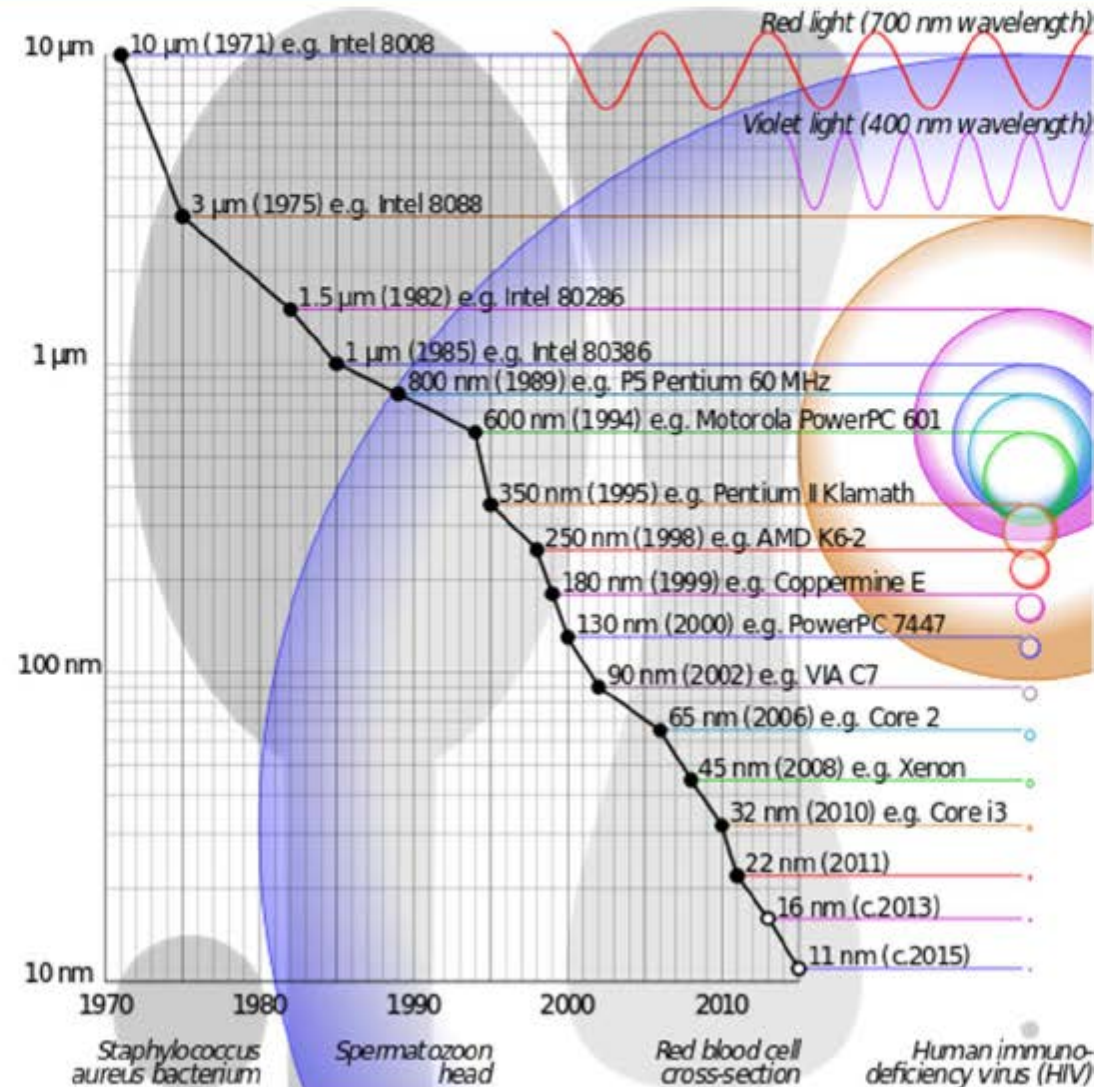

32 nm technology (2010)

- Intel's Core i3, i5, i7 processors

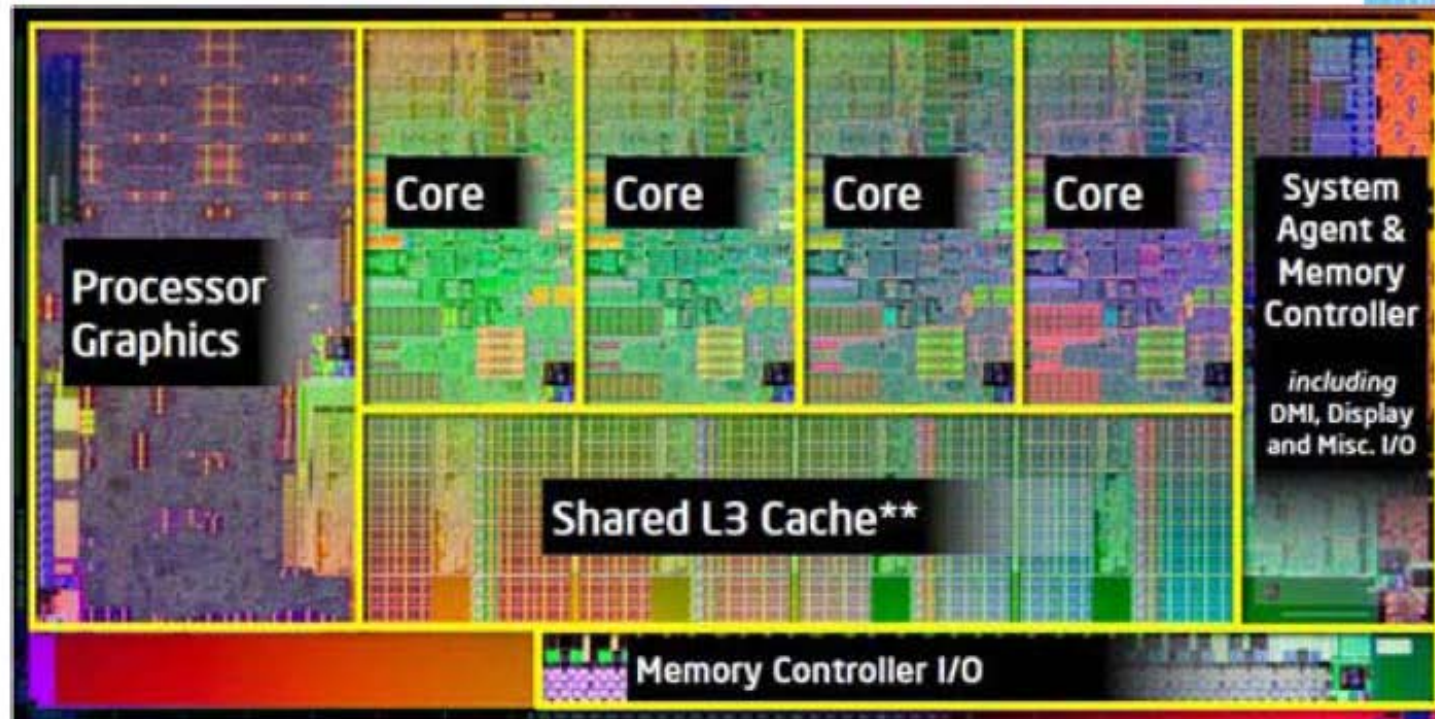

Powerful Roadmap with Rapid Innovation

Continued Ampere Innovation Leads to Breakaway Performance Using Unique Architecture

2020

2021

2022

2023

2024

2025

2026

Ampere® Altra® Family

Up to 80 Cores
7nm

Up to 128 Cores
7nm



8-Channel DDR4

AmpereOne® Family

Up to 192 Cores
5nm

Up to 256 Cores
3nm







8-Channel DDR5

12-Channel DDR5

Generally Available

Ready at Fab

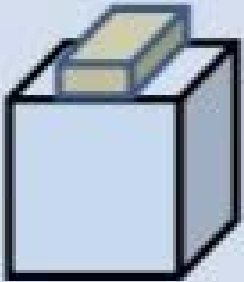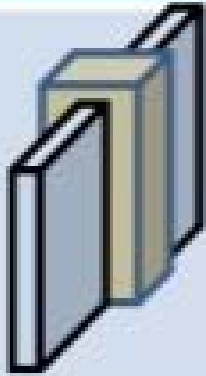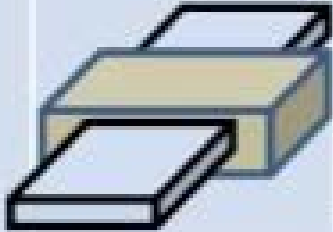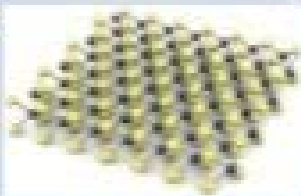Type	Bulk	FinFET	Nano-sheet	2D-TMD	Nano-wire	CNT
Structure						
L_{MIN}^* (nm)	25-30	2.5-3 W_{FIN}	$2.5 T_{\text{CH}}$	$2.5 T_{\text{CH}}$	1.5 d_{W}	1.5 d_{CNT}

About electronics ...

- Electronics is everywhere
 - A field at the leading edge of technology, with rapid rate of progress
 - Pushes the limits in speed, degree of integration, automation ...
-

After this course, you'll be able to ...


- **Calculate** conduction properties of materials and simple device structures
 - **Explain** the operating principles of semiconductor diodes and FETs
 - **Determine** the in-circuit operating state of diodes and FETs
 - **Perform** large signal analysis of circuits containing diodes and FETs
 - **Use** a modern schematic capture and computer-aided circuit analysis program (SPICE)
 - **Calculate** the performance parameters for different MOS logic families to design and build circuits
-

Devices and Circuits I

Circuit Theory Review

- Starting point:
 - Ohm's Law (OL)
 - Kirchhoff's voltage law (KVL)
 - Kirchhoff's current law (KCL)
 - Derive:
 - Voltage Division
 - Current Division
 - Thevenin Equivalent Circuits
 - Norton Equivalent Circuits
-

Voltage Division

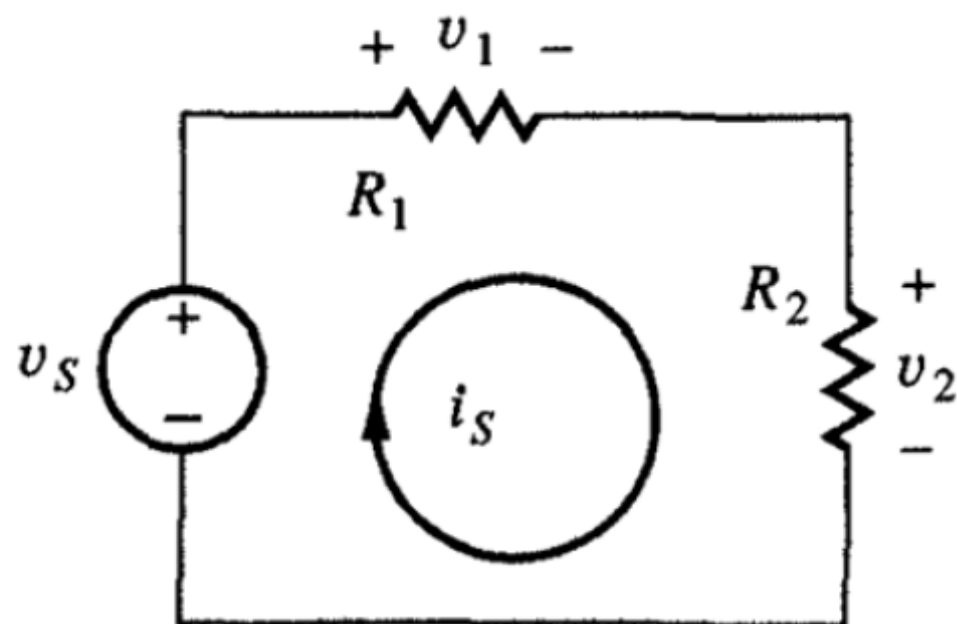

$$\text{OL: } v_1 = i_s R_1$$

$$\text{OL: } v_2 = i_s R_2$$


$$\begin{aligned} \text{KVL: } v_s &= v_1 + v_2 \\ &= i_s(R_1 + R_2) \end{aligned}$$



$$v_1 = v_s \frac{R_1}{R_1 + R_2}$$

$$v_2 = v_s \frac{R_2}{R_1 + R_2}$$

Current Division

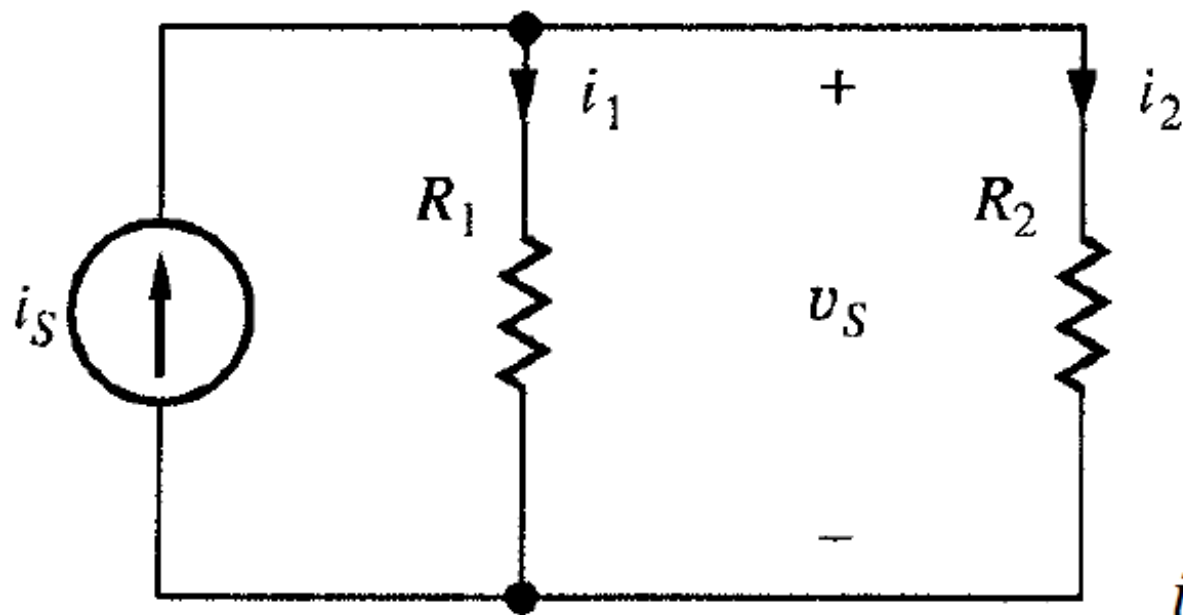

$$\text{OL: } i_1 = \frac{v_S}{R_1}$$

$$\text{OL: } i_2 = \frac{v_S}{R_2}$$

$$\begin{aligned} \text{KCL: } i_S &= i_1 + i_2 \\ &= \frac{v_S}{R_1} + \frac{v_S}{R_2} = \frac{v_S}{(R_1 || R_2)} \end{aligned}$$




$$i_1 = i_S \frac{R_1 || R_2}{R_1} = i_S \frac{R_2}{R_1 + R_2}$$


$$i_2 = i_S \frac{R_1 || R_2}{R_2} = i_S \frac{R_1}{R_1 + R_2}$$

Thevenin Equivalent Circuits

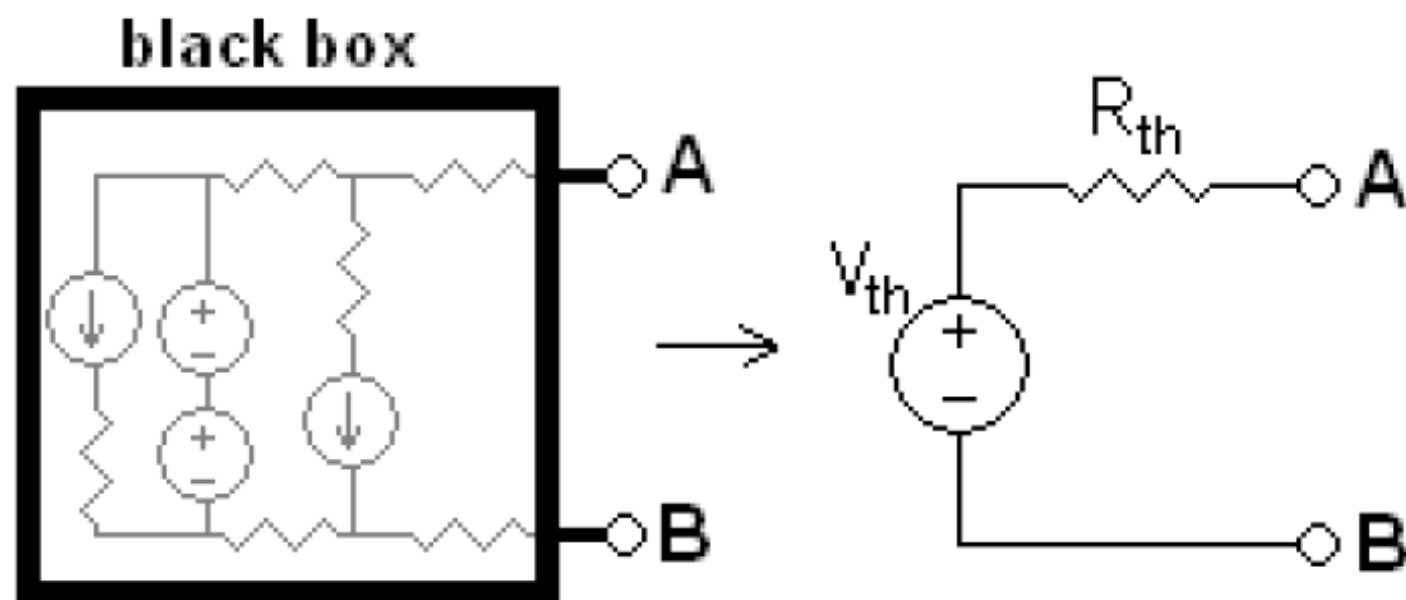- Voltage source V_{Th} is the **open circuit** voltage at the output terminals
- R_{Th} : equivalent resistance present at the output terminals with all **independent** sources **set to zero**



Thevenin Equivalent Circuits (e.g. 1)

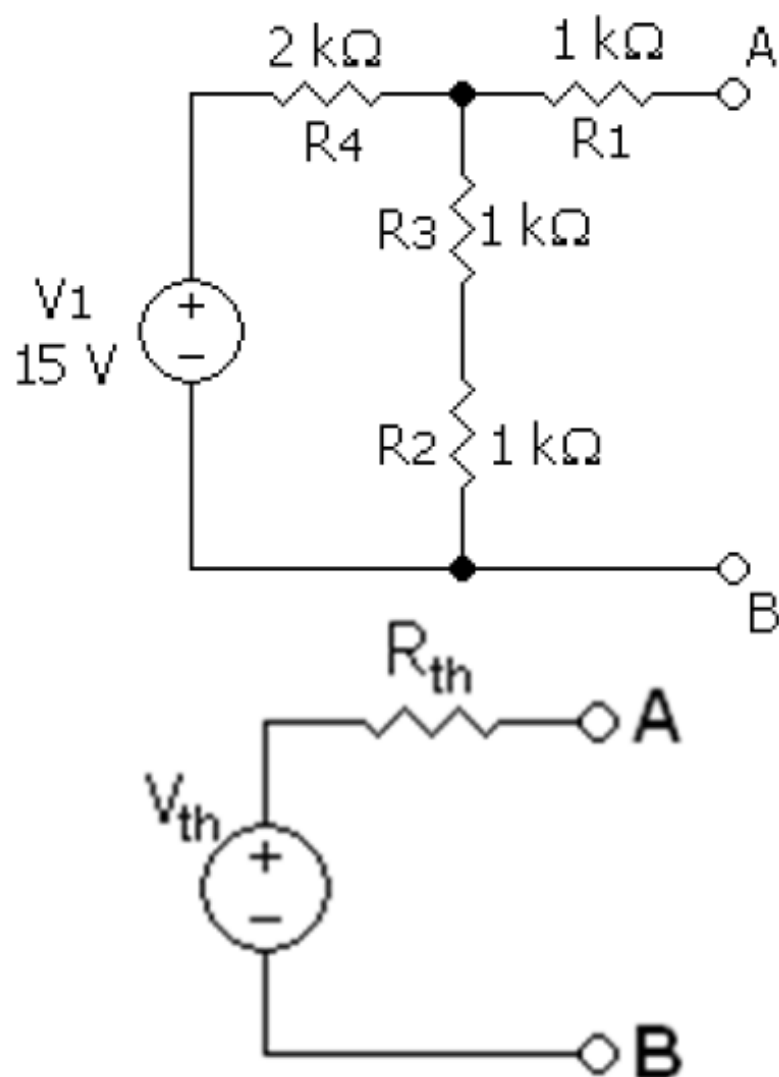



Open circuit voltage:

$$V_{Th} = V_{23} \quad \text{voltage division}$$
$$= V_1 \frac{R_4}{R_4 + R_2 + R_3} = 7.5\text{ V}$$

Set V_1 to zero.

$$R_{Th} = R_1 + R_4 || (R_2 + R_3)$$
$$= 1\text{ k}\Omega + 2\text{ k}\Omega || 2\text{ k}\Omega = 2\text{ k}\Omega$$

Thevenin Equivalent Circuits (e.g. 2)

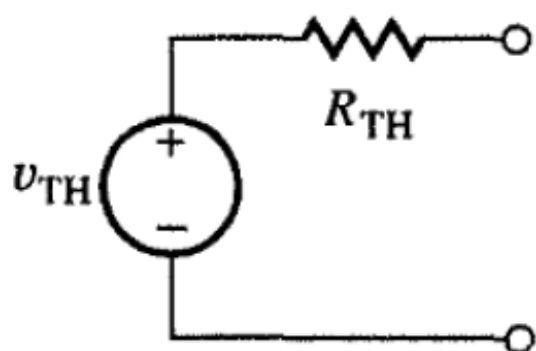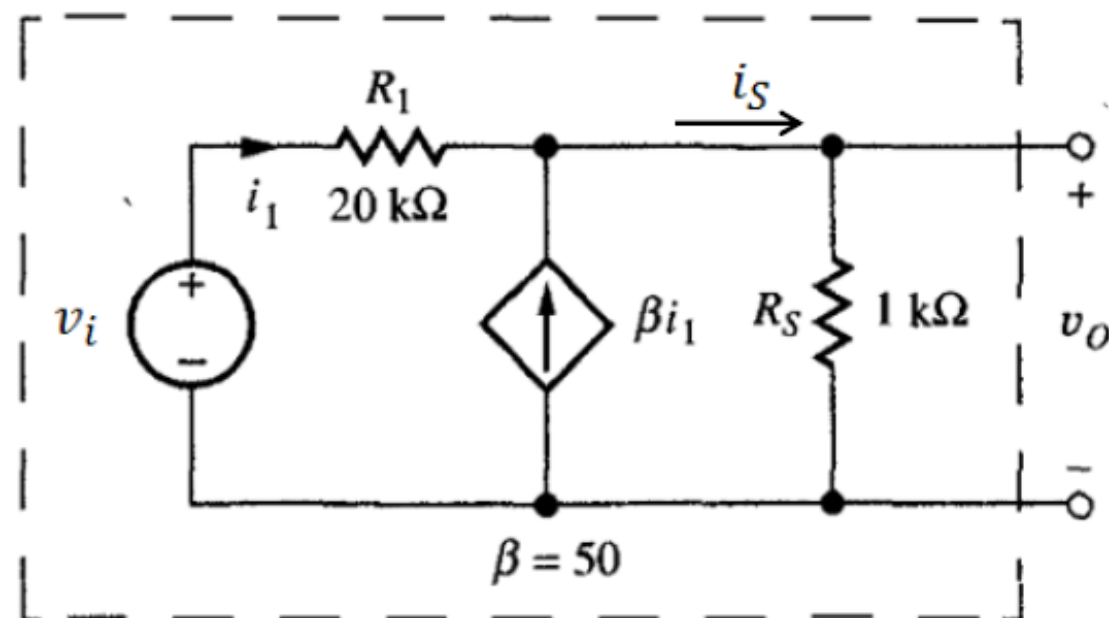

$$V_{Th} = i_S R_S$$

$$\text{KCL: } i_S = (1 + \beta) i_1$$

$$\Rightarrow V_{Th} = (1 + \beta) i_1 R_S$$


KVL:

$$v_i = i_1 R_1 + (1 + \beta) i_1 R_S$$



$$V_{Th} = v_i \frac{(1 + \beta) R_S}{R_1 + (1 + \beta) R_S}$$

Thevenin Equivalent Circuits (e.g. 2)

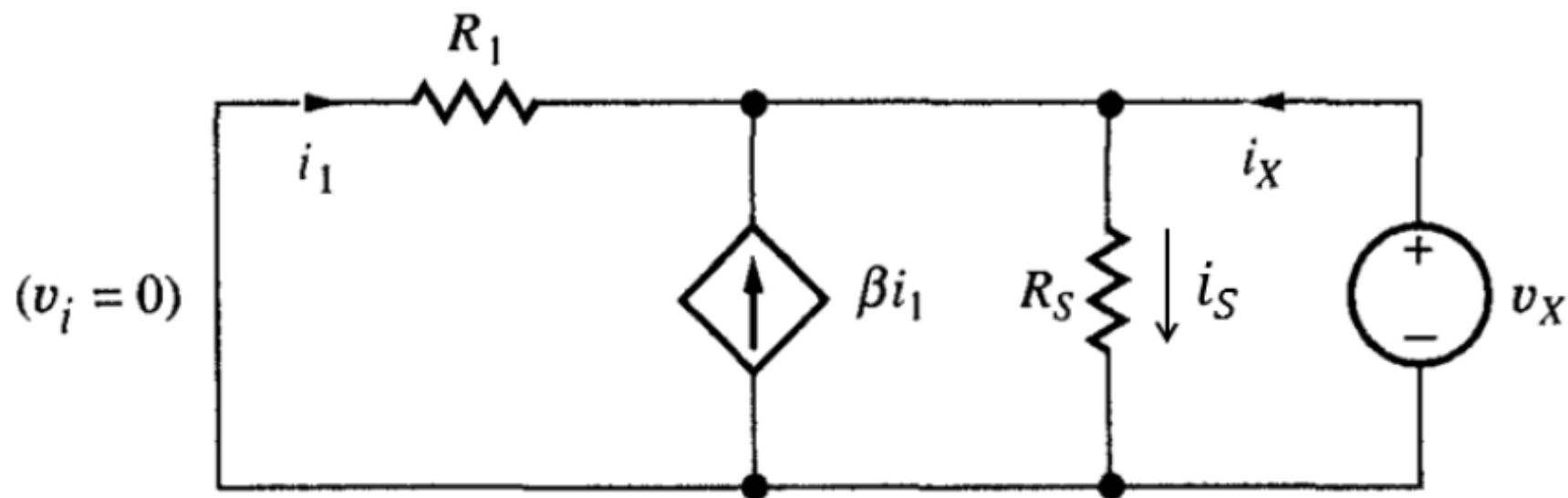

KVL: $v_X = -i_1 R_1$; $v_X = i_S R_S$


KCL: $i_S = i_X + (1 + \beta)i_1$

$$\Rightarrow v_X = [i_X + (1 + \beta)i_1]R_S = \left[i_X - (1 + \beta)\frac{v_X}{R_1} \right] R_S$$

$$\Rightarrow R_{Th} = \frac{v_X}{i_X} = v_S \frac{R_S}{1 + (1 + \beta)R_S/R_1}$$


Norton Equivalent Circuits

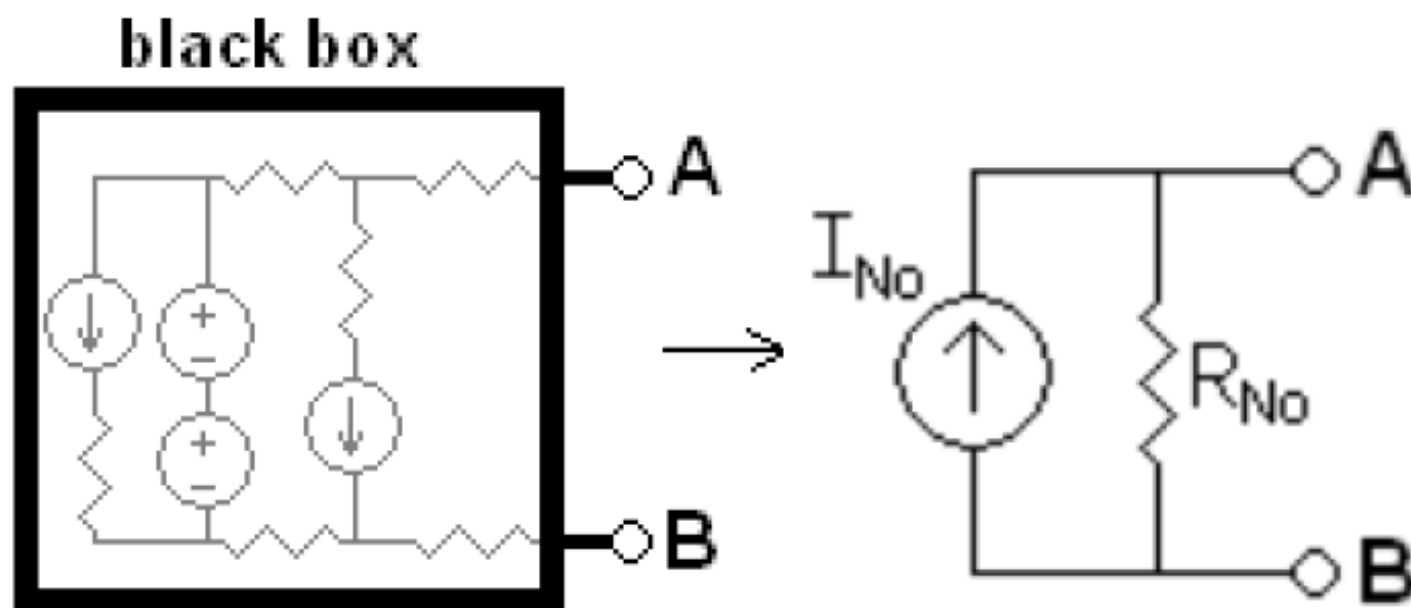- I_{No} : current coming out of the network when terminals are **shorted**
- R_{No} : equivalent resistance present at the output terminals with all **independent** sources **set to zero** ($R_{No} = R_{Th}$)




Norton Equiva

Find Norton equivalent I_n and R_n

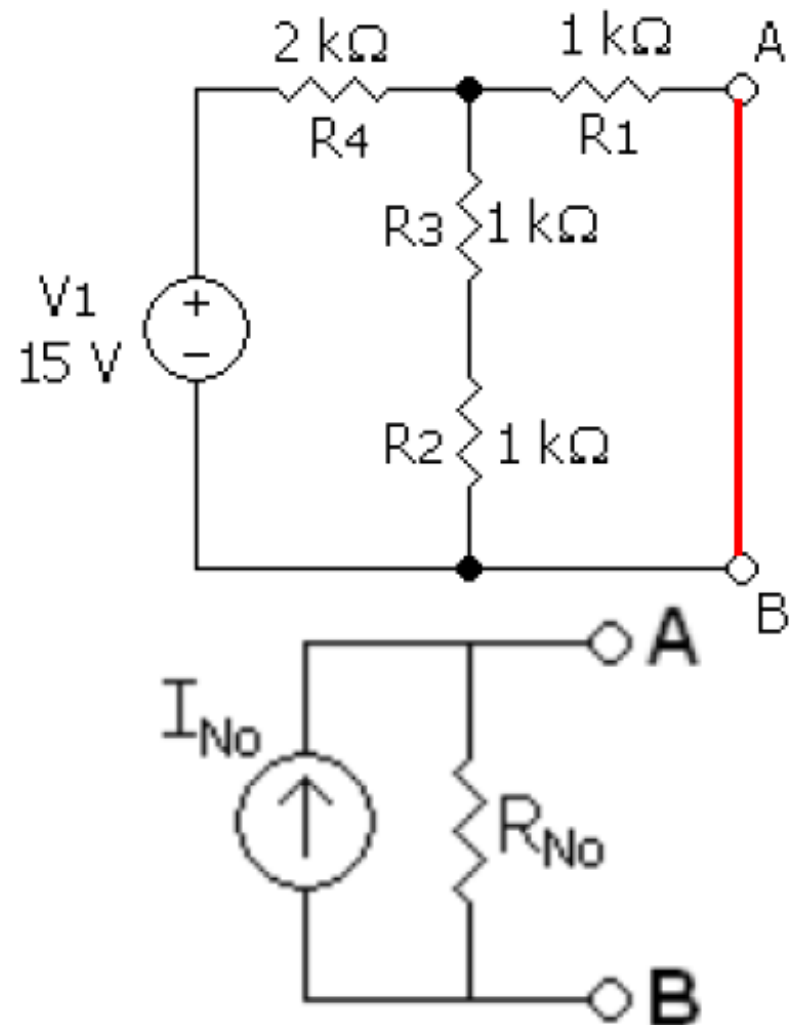

Norton Equivalent Circuits (e.g. 1)

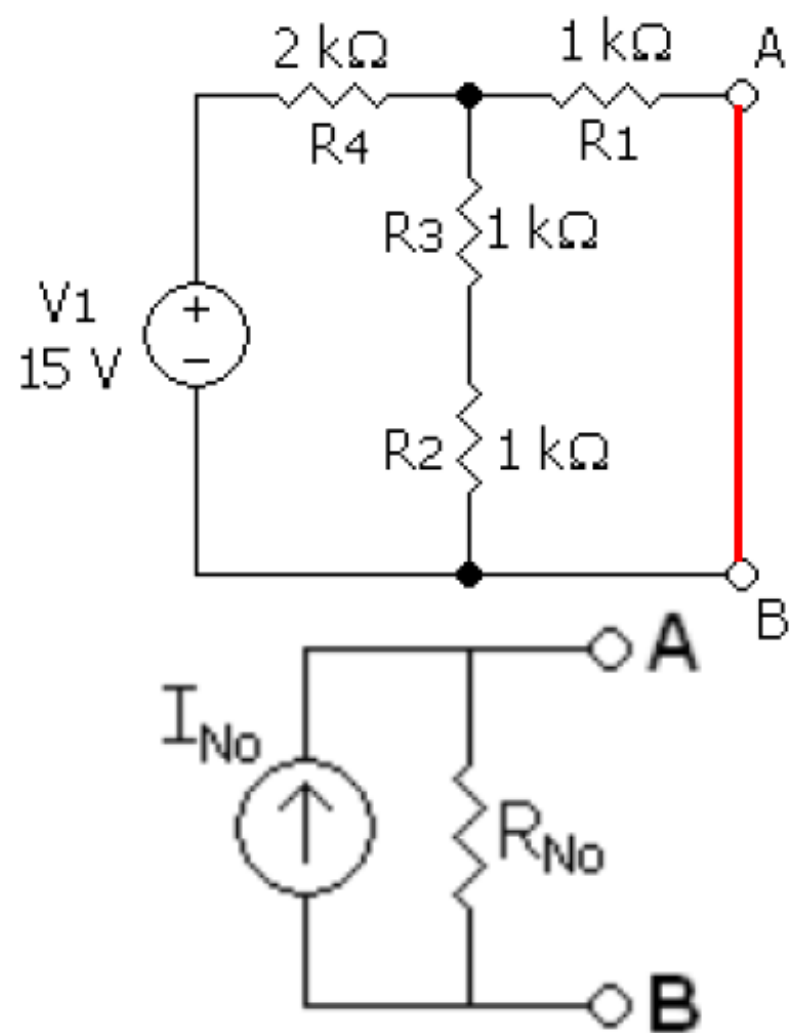

$$i_{tot} = \frac{V_1}{R_{tot}} = \frac{V_1}{R_4 + R_1 || (R_2 + R_3)} = 5.63 \text{ mA}$$

Short Circuit current:




$$I_{No} = i_{tot} \frac{R_2 + R_3}{R_2 + R_3 + R_4} = 3.75 \text{ mA}$$

current division

Set V_1 to zero.

$$\begin{aligned} R_{No} &= R_1 + R_4 || (R_2 + R_3) \\ &= 1 \text{ k}\Omega + 2 \text{ k}\Omega || 2 \text{ k}\Omega = 2 \text{ k}\Omega \end{aligned}$$

Norton Equivalent Circuits (e.g. 2)

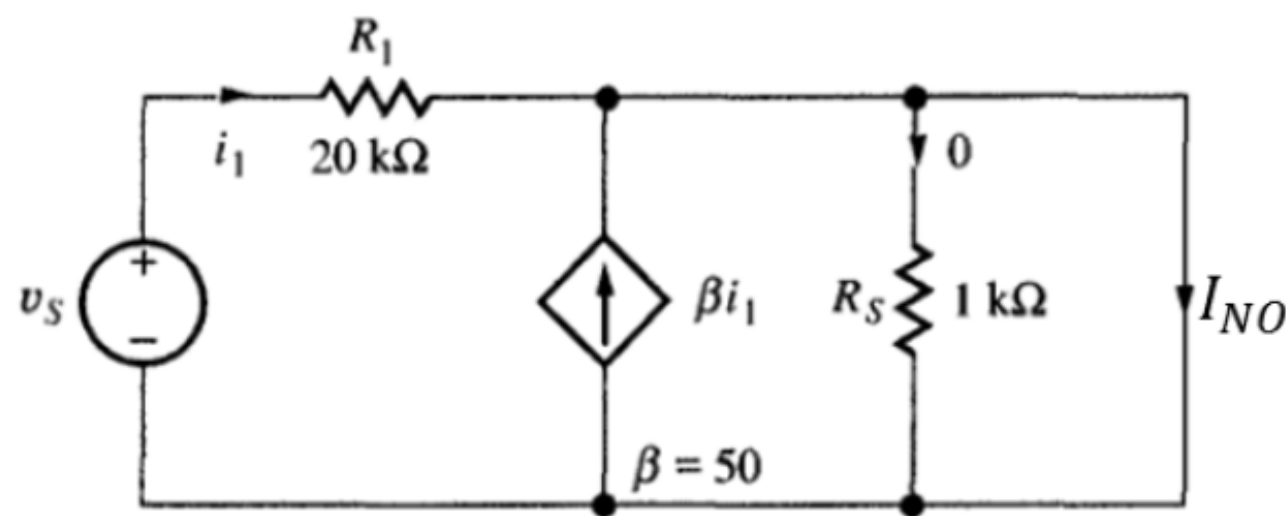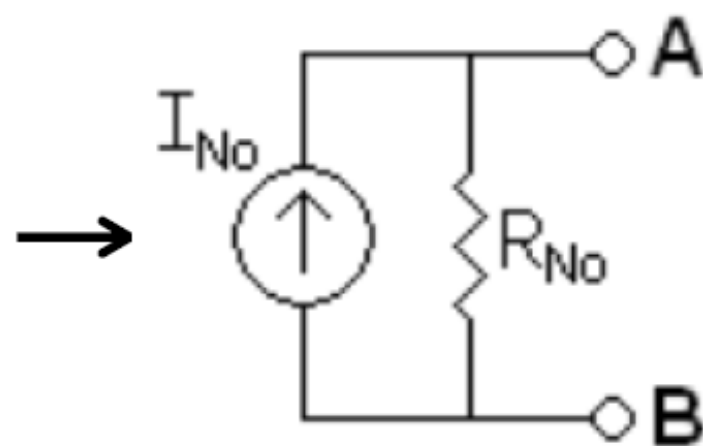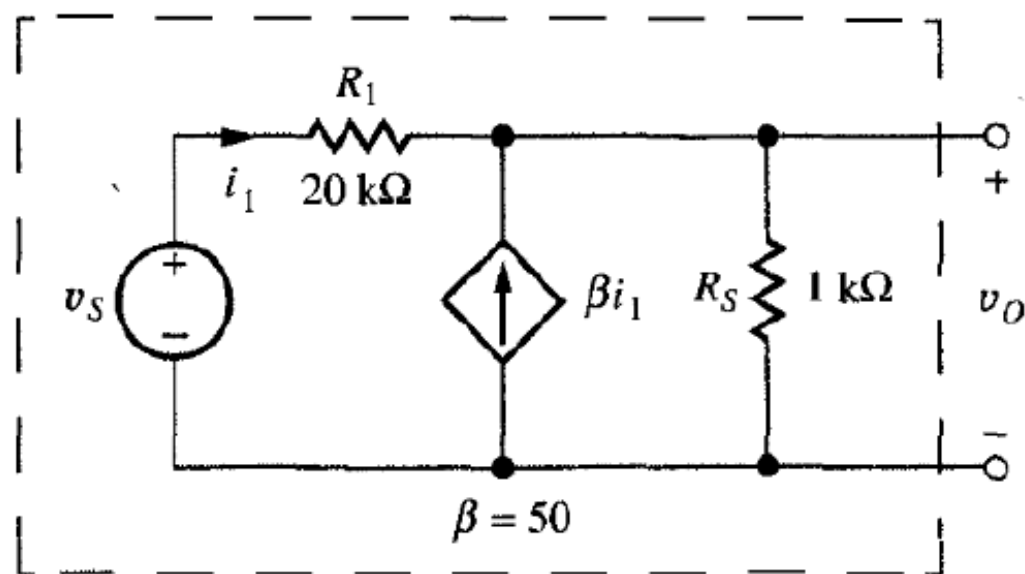

$$I_{No} = (1 + \beta)i_1 \\ = (1 + \beta)v_S/R_1$$

R_{No} is the same as R_{Th} in Thevenin equivalent circuits

$$V_{Th} = I_{No}R_{Th}$$